



Inspiring Excellence

CSE260: Digital Logic Design


Summer 2025

Quiz - 02

Duration: 30 minutes

A


Name:	ID:	Section:
-------	-----	----------

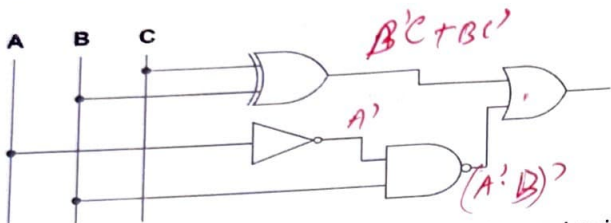1.CO2	 <p>a. Determine the Logic function of the above circuit. b. Simplify the function you obtained in part(a) using Boolean algebra</p>	5
2.CO2	Convert the Boolean function to its Canonical POS form. $F(A,B,C) = C' + A \oplus B$	5
3.CO2	$F(A,B,C,D) = \Sigma(0,2,4,5,6,7,8,9,10,14)$ Use Karnaugh Map to find the simplified expression.	5

1) a)  $(A'B)' + B'C + BC'$   
 b)  $A + B' + B'C + BC'$   
 $= A + B'(1+C) + BC'$   
 $= A + B' + BC'$   
 $= A + (B'+B)(B'+C')$   
 $= A + B' + C'$

2)  $F = C' + A \oplus B$   
 $= C' + A'B + AB'$   
 $= (C' + A'B + A)(C' + A'B + B')$   
 $= (A + C' + A')(A + C' + B)(B' + C' + A')$   
 $(B' + C' + B)$   
 $= (A + B + C')(A' + B' + C')$   
 $= 001, 111$   
 $= \pi(1, 7)$

3)

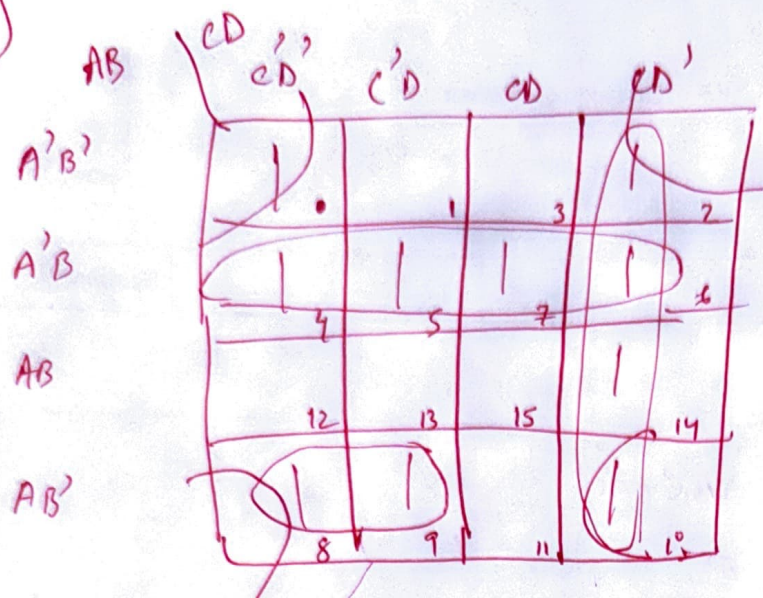

$$F = A'B + CD + AB'C' + B'D'$$

\* Alternate Solution is possible-