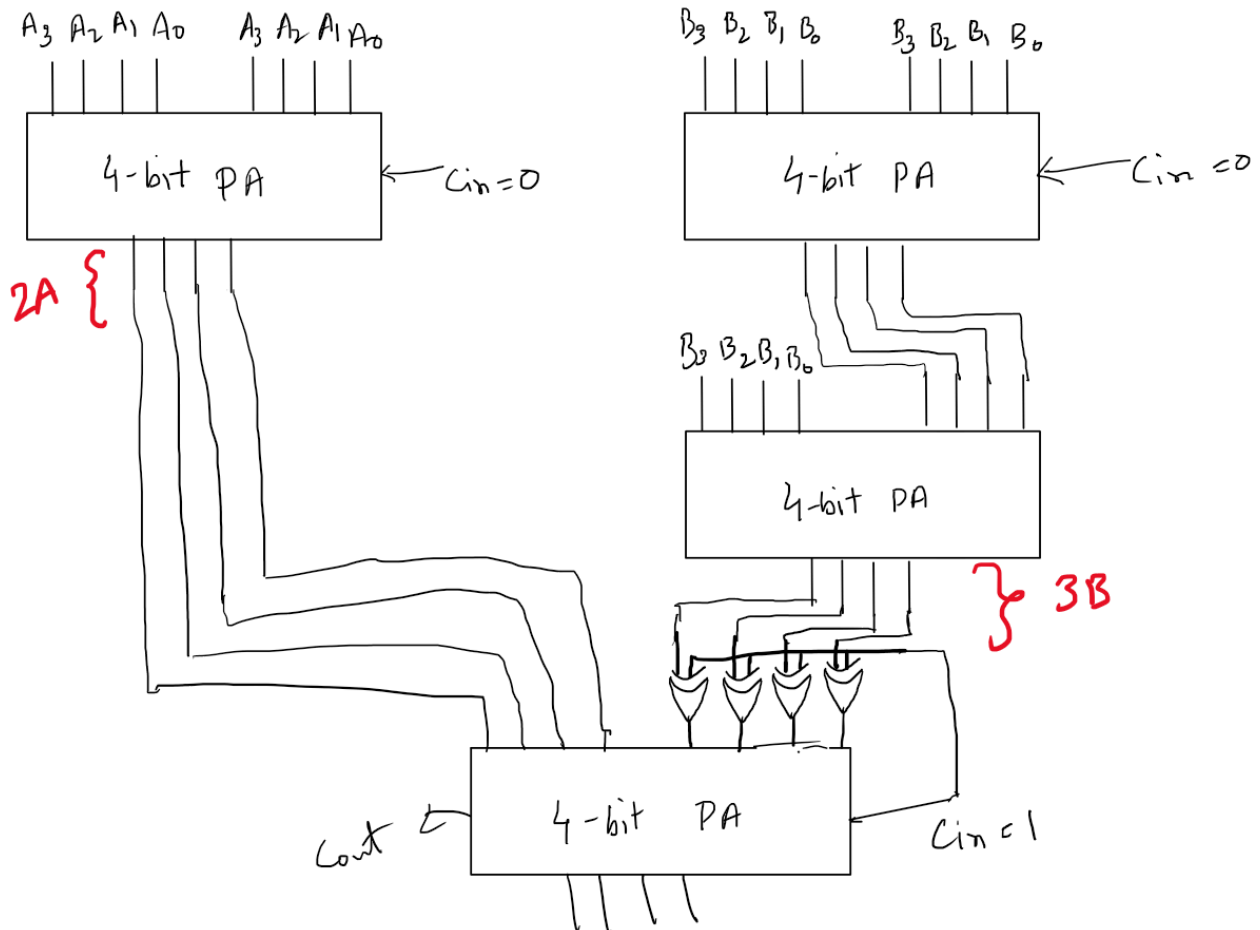


Name:	ID:	Section:
-------	-----	----------

1.	Design a circuit that produces (2A - 3B) using 4-bit parallel adders. Assume the value of 2A and 3B to be within 4-bit numbers. Use external gates if necessary.	10
2.	A RAM is constructed using a 11x2048-size decoder with 24 binary cells per word. <ol style="list-style-type: none"> How many words does the memory hold? How many flip-flops are needed in the MBR? How many address lines are needed? How many flip-flops are required in the MAR? What is the total capacity of this RAM in KB? 	5



2.

a. 2048

b. 24

c. 11

d. 11

e. Capacity = $2048 \times 24 = 49152$ bits / $8 \times 1024 = 6$ KB