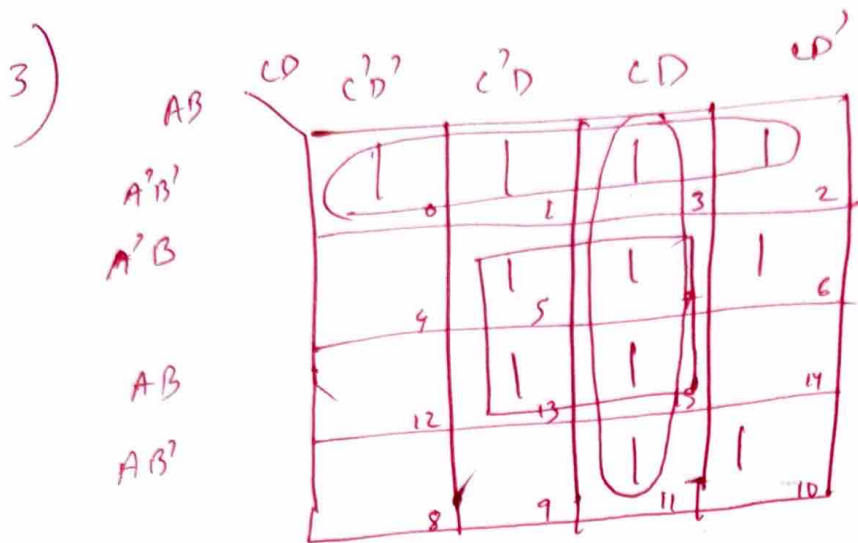


Name:	ID:	Section:
-------	-----	----------


1.CO2	<p>a. Determine the Logic function of the above circuit. b. Simplify the function you obtained in part(a) using Boolean algebra</p>	5
2.CO2	Convert the Boolean function to its Canonical POS form. $F(A,B,C) = C' + A \oplus B$	5
3.CO2	$F(A,B,C,D) = \sum(0,1,2,3,5,6,7,10,11,13,15)$ Use Karnaugh Map to find the simplified expression.	5

1) a) $A + (AB + C')'$
b) $A + \overline{AB} \cdot C$
 $= A + (\overline{A} + \overline{B}) \cdot C$
 $= A + \overline{A}C + \overline{B}C$
 $= (A + \overline{A})(A + C) + \overline{B}C$
 $= A + C + \overline{B}C$
 $= A + C + \overline{B}C$
 $= A + C(1 + \overline{B})$
 $= A + C$

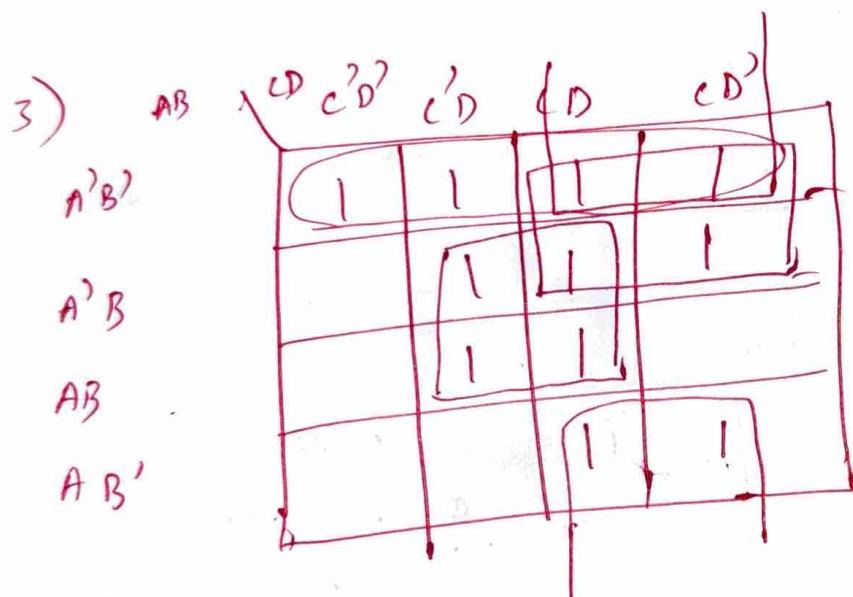2) $F = C' + A \oplus B$
 $= C' + A'B + AB'$
 $= (C' + A'B + A)(C' + A'B + B')$
 $= (A + C' + A')(A + C' + B)(B' + C' + A')$
 $= (A + B + C')(A' + B' + C')$
 $= 001, 111$
 $= \pi(1, 7)$



\Rightarrow This approach
will take
5 groups



\Rightarrow This approach
will take
4 groups

$$F = A'B' + BD + A'C + B'C$$