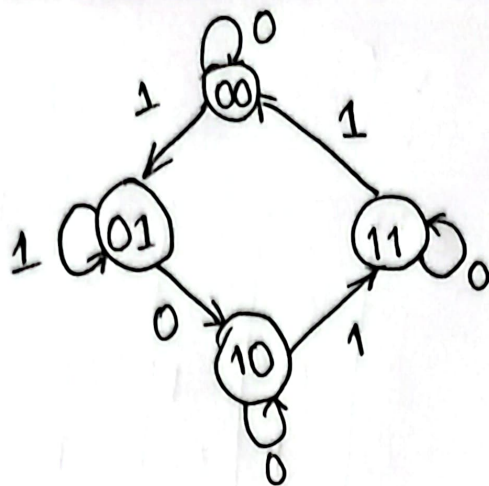




Present state		Input X	Next state		Flip flop input			
A	B		A ⁺	B ⁺	SA	RA	SB	RB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	0
0	0	0	1	0	1	0	0	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	0
1	1	0	1	1	X	0	X	0
1	1	1	0	0	0	1	0	1

SR Flip flop
truth table

S	R	Q	Q'
0	0	No change	
0	1	0	1
1	0	1	0
1	1	Not used	

SR excitation table

Q	Q ⁺	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR flip flop,
characteristic table

Q(t)	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Indeterminant
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Indeterminant

$$SA = B\bar{x}$$

A \ Bx	00	01	11	10
0				1
1	X	X		X

$$SB = \bar{B}x$$

A \ Bx	00	01	11	10
0		1	X	
1		1		X

$$RA = Bx$$

A \ Bx	00	01	11	10
0	X	X	X	
1			1	

$$RB = ABx + A'x$$

A \ Bx	00	01	11	10
0	X			1
1	X		1	

